

List of Figures

1.1	Results of a survey on the causes of power quality problems. (Courtesy of Georgia Power Co.)	8
1.2	Basic steps involved in a power quality evaluation.	11
1.3	Switch-mode power supply.	20
1.4	SMPS current and harmonic spectrum.	21
1.5	Fluorescent lamp with (a) magnetic ballast current waveform and (b) its harmonic spectrum.	23
1.6	Fluorescent lamp with (a) electronic ballast current waveform and (b) its harmonic spectrum.	25
1.7	Current and harmonic spectrum for CSI-type ASD.	27
1.8	Current and harmonic spectrum for PWM-type ASD.	28
1.9	Six-pulse dc ASD.	29
1.10	PWM ASD	30
1.11	Large ac ASDs	30
1.12	Effect of PWM ASD speed on ac current harmonics.	31
1.13	Equivalent circuit for an arcing device.	32
1.14	Transformer magnetizing Characteristic	33
2.1	12 pulse converter	44
2.2	Active/Reactive Power Locus for symmetrical Firing angle operation . . .	45
2.3	Active Power vs Reactive power	46
2.4	Effect of Overlap angle on Firing angle	48
2.5	3-D Plot of active power with simultaneous variation in converter 1 and converter 2 firing angles without source inductance	49

2.6	3-D Plot of active power with simultaneous variation in converter 1 and converter 2 firing angles with source inductance	50
2.7	3-D Plot of reactive power with simultaneous variation in converter 1 and converter 2 firing angles without source inductance	51
2.8	3-D Plot of reactive power with simultaneous variation in converter 1 and converter 2 firing angles with the effect of source inductance	52
2.9	Limiting firing angles of operation of 12- pulse converter at $\mathbf{q}_{set} \geq \mathbf{q}_{mid}$. .	54
2.10	Limiting firing angles of operation of 12- pulse converter at $\mathbf{q}_{set} \leq \mathbf{q}_{mid}$. .	54
2.11	Range of firing angles for constant reactive power operation with source inductance	56
2.12	Range of firing angles for constant reactive power operation with source inductance	56
2.13	Range of firing angles for constant reactive power operation with source inductance effect.	57
2.14	Range of firing angles for constant reactive power operation with variation in I_d	57
2.15	Range of firing angles for constant reactive power operation with variation in I_d	58
2.16	Limiting Firing angle operation of 12- pulse converter for P_{set} value	58
2.17	Range of firing angles for constant Active power	60
2.18	Range of firing angles for constant Active power	60
2.19	Active power Vs Converter 2 firing angle	61
2.20	Reactive power Vs Converter 2 firing angle	62
2.21	per unit 5^{th} , 7^{th} , 11^{th} and 13^{th} harmonics for simultaneous variation of converter 1 and 2 firing angles	66
2.22	% THD 5^{th} , 7^{th} , 11^{th} and 13^{th} harmonic component Vs Converter 2 firing angle	67
2.23	waveform for equal firing angle	68
2.24	waveform for equal firing angle	68
2.25	waveform for unequal firing angle	69
3.1	Passive Filter	71
3.2	Single Tuned Filter	73

3.3	High Pass Filter	75
3.4	Double Tuned Filter	76
3.5	Double Tuned High Pass Filter	78
3.6	Triple Tuned Filter	80
3.7	Asymptotes and pass band plot	86
3.8	Active power V/s Converter 2 firing angle with converter 1 firing angle constant.	88
3.9	Active power V/s Converter 2 firing angle with converter 1 firing angle constant.	89
3.10	Reactive power V/s Converter 2 firing angle with converter 1 firing angle constant	90
3.11	Reactive power V/s Converter 2 firing angle with converter 1 firing angle constant	91
3.12	% Harmonics V/s Converter 2 firing angle with converter 1 firing angle constant	92
3.13	% Harmonics V/s Converter 2 firing angle with converter 1 firing angle constant	93
3.14	Active power v/s Reactive power and combination of firing angle.	94
3.15	harmonic components for equal firing angle	95
3.16	harmonic components for equal firing angle	95
3.17	harmonic components for equal firing angle	96
3.18	harmonic components for unequal firing angle	96
4.1	Shunt active filter	100
4.2	Hybrid series active filter_1	101
4.3	Hybrid series active filter_2	101
4.4	Equivalent Circuit	103
4.5	Harmonic Equivalent Circuit	103
4.6	Clarke transformation	107
4.7	Physical meaning of p & q	109
4.8	Components of p, q and p0	109
4.9	Current compensation based on p-q theory	110
4.10	Hysteresis current control	111

4.11 HAF for 12 pulse converter	112
4.12 Both converter firing angle 30 degree	112
4.13 Both converter firing angle 40 degree	113
4.14 Converter 1 at 30degree and converter 2 at 60 degree	115
4.15 Block diagram of synchronous reference frame theory algorithm	115
4.16 Both converters are at 0 degree firing angle	117
4.17 Both converters are at 50 degree firing angle	118
4.18 converter 1 at o degree and converter 2 at 30 degree	119
4.19 Converter 1 at 10 degree and converter 2 at 30 degree	120
4.20 Change in firing angle at $t = 0.08$ sec.	122
4.21 Change in firing angle at $t=0.08$ second and variation in dc voltage for six pulse and Twelve pulse converter	123
4.22 Insertion and removal of HAF at $t=0.06$ sec. and at $t =0.12$ sec. respectively	123
4.23 Load pertibutation at $t = 0.06$ sec.	124
4.24 Load perturbation at unequal firing angle	125
4.25 Effect of converter firing angle on Active power	127
4.26 Effect of converter firing angle on Active power	128
4.27 Effect of converter firing angle on Reactive power	129
4.28 Effect of converter firing angle on Reactive power	130
4.29 % THD Vs Converter 2 firing angle by keeping converter 1 firing angle constant for 12 pulse converter with and without active and passive filter.	131
4.30 % THD Vs Converter 2 firing angle by keeping converter 1 firing angle constant for 12 pulse converter with and without active and passive filter.	132
4.31 Effect on harmonic components for firing angle of Converter 2	134
4.32 Effect on harmonic components for firing angle of Converter 2	135
4.33 Combiend hybrid active filter	135
4.34 comparison of supply current harmonics	136
4.35 comparison of supply voltage harmonics	136
5.1 Power circuit diagram for 12 pulse converter	139
5.2 Six pulse converter star star connected	139
5.3 Six pulse converter star- delta connected	140
5.4 Equal firing angle mode	141

5.5	Unequal firing angle mode	142
5.6	The view of DSP F2812 kit	145
5.7	Flow chart	146
5.8	General arrangement	148
5.9	Current and voltage sensors CTs & PTs along with waveforms	149
5.10	Signal conditioning circuit with waveforms	149
5.11	Control signals of 3.3 V & 5 V with dead time.	150
5.12	Inverter module	150
5.13	Supply current waveform with HAF	151